

Str. 126 / uloha 642

$$k = \frac{2}{15}$$

$$U_1 = 600V$$

$$U_2 = ? [V]$$

$$\boxed{k = \frac{U_2}{U_1}}$$

\Rightarrow

$$U_2 = k \cdot U_1$$

$$U_2 = \frac{2}{15} \cdot 600$$

$$\underline{\underline{U_2 = 80V}}$$

Na sekundárni cívce transformátora je 80 V.